

Lab: AC Problems 1

Name_____ Per_____

Remember that μf is $1 \times 10^{-6} \text{ F}$
and the Formulae are in your Notes!

	<u>Find</u>	<u>When</u>	<u>Answer</u>
1.	X_L	$f = 400 \text{ Hz}$ $L = 20 \text{ h}$	$50,000 \ \Omega$
2.	X_C	$f = 60 \text{ Hz}$ $C = 20 \ \mu\text{F}$	$1.3 \times 10^2 \ \Omega$
3.	Z	$X_L = 50 \ \Omega$ $X_C = 100 \ \Omega$ $R = 500 \ \Omega$	$502 \ \Omega$
4.	I	$V = 200 \text{ v}$ $Z = 800 \ \Omega$	0.25 a
5.	$f_{(\text{resonant})}$	$L = 20 \text{ h}$ $C = 40 \ \mu\text{F}$	5.7 Hz